
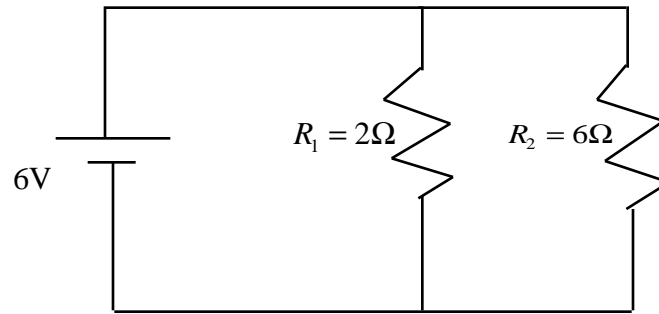


## PARALLEL CIRCUITS – QUIZ 23a

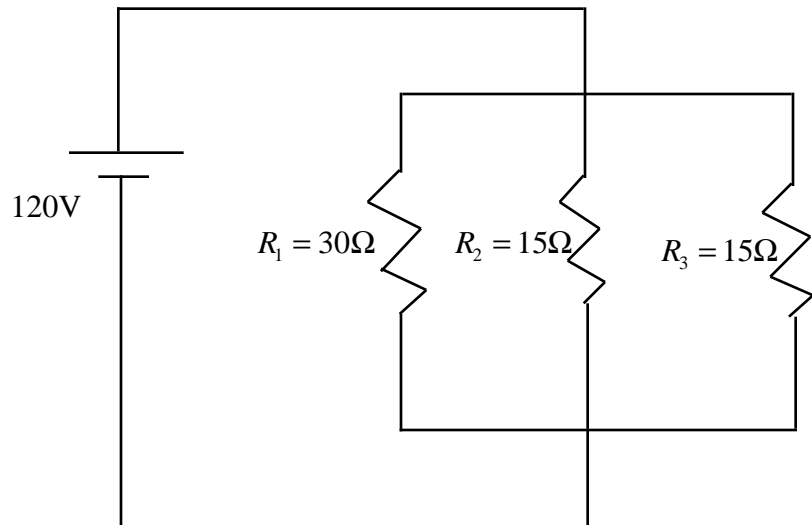1. (a) Find  $R_T$   
(b) Find  $I_T$   
(c) Find  $I_1$  and  $I_2$   
(d) Find  $V_1$  and  $V_2$



2. (a) Find  $R_T$   
(b) Find  $I_T$   
(c) Find  $I_1$ ,  $I_2$  and  $I_3$   
(d) Find  $V_1$ ,  $V_2$  and  $V_3$



3. (a) Find  $R_T$   
(b) Find  $V_T$   
(c) Find  $I_1$  and  $I_2$   
(d) Find  $V_1$  and  $V_2$

